

HPAD 0.2 Submission - Bonn

H. Krüger

Overview

- Motivation
- Implemented structures (test chip including 4 different developments)
 - switch test structures
 - 8 cell analog pipeline
 - I²C interface (not connected to the above)
 - tripple-well nfet (*nfettw*) test structures
- Pipeline issues
- General remarks

Motivation

- HPAD 0.1 switch test structures all *DGPFET* (thick gate oxide, 2.5V, reg. V_t)
- favorite device because:
 - no gate leakage
 - low off-current
 - sustain higher dynamical range (2.5V instead of 1.5V)

But, too bad:

- HPAD 0.1 irradiation results showed high V_{th} shift (< 700mV after 10MGy)
- Unless dose rate effect is not significant (is it?) we cannot use this type of transistor

Switch Design Challenges

- charge up the sampling capacitor within 200 ns sampling time
- store the voltage during 100ms (worst case) hold time
- do both with an error of less than 0.1% (1%)

settling time constant: $C_S \cdot r_{ON} = 28\text{ns}$ (43ns)

hold time constant: $C_S \cdot r_{OFF} = 20\text{s}$ (2s)

→ ratio $r_{ON}/r_{OFF} = 7 \cdot 10^8$ ($4 \cdot 10^7$) !

Differences HPAD 0.1 \leftrightarrow HPAD 0.2

On HPAD 0.1 there were two different type of structures to study device leakage


1. devices arrays (switches and capacitors)
 - many **devices in parallel** to make ultra low current measurements feasible (O(1000) devices, sub pA per device)
 - measure dc currents (**V-I curves**)
2. sampling cells
 - combination of switch, capacitor and buffer
 - measure (**time dependent**) voltage drop on sampling capacitor

New switch test structures are implemented as sampling cells

- **DGNCAP** capacitors (showed negligible leakage current on HPAD 0.1)
- Zero-VT **DGNFET source follower**
- different **PFET** (thin gate oxide) switch configurations


HPAD 0.2 Switch Test Structures

 - Sampling cells, 8 variants:
 - all **LPPFET** (low power, high V_T):
 - single (w/o M2) or dual switch configurations
 - W/L variations
 - **enclosed** and **linear**
 - $6\mu\text{x}6\mu$ **DGNCAP** ($\geq 200\text{fF}$, non-linear!) capacitor



Cell #	Enc.	D/S	V_{THR}	W/L	NWELL	SD	Comments
1	Y	S	LP	2.24/0.12	external	-	$W_{min} = 2.24$ for enc. layout
2	Y	S	LP	2.24/0.24	external	-	
3	Y	S	LP	2.24/0.36	external	-	
4	N	S	LP	0.32/0.12	external	-	
5	N	S	LP	0.64/0.12	external	-	
6	N	S	LP	0.64/0.24	external	-	
7	N	D	LP	0.64/0.12 (both)	external	external	
8	N	D	LP	0.64/0.12 (both)	-	-	$V_{SD} = V_{NWELL}$


HPAD 0.2 Switch Test Structures

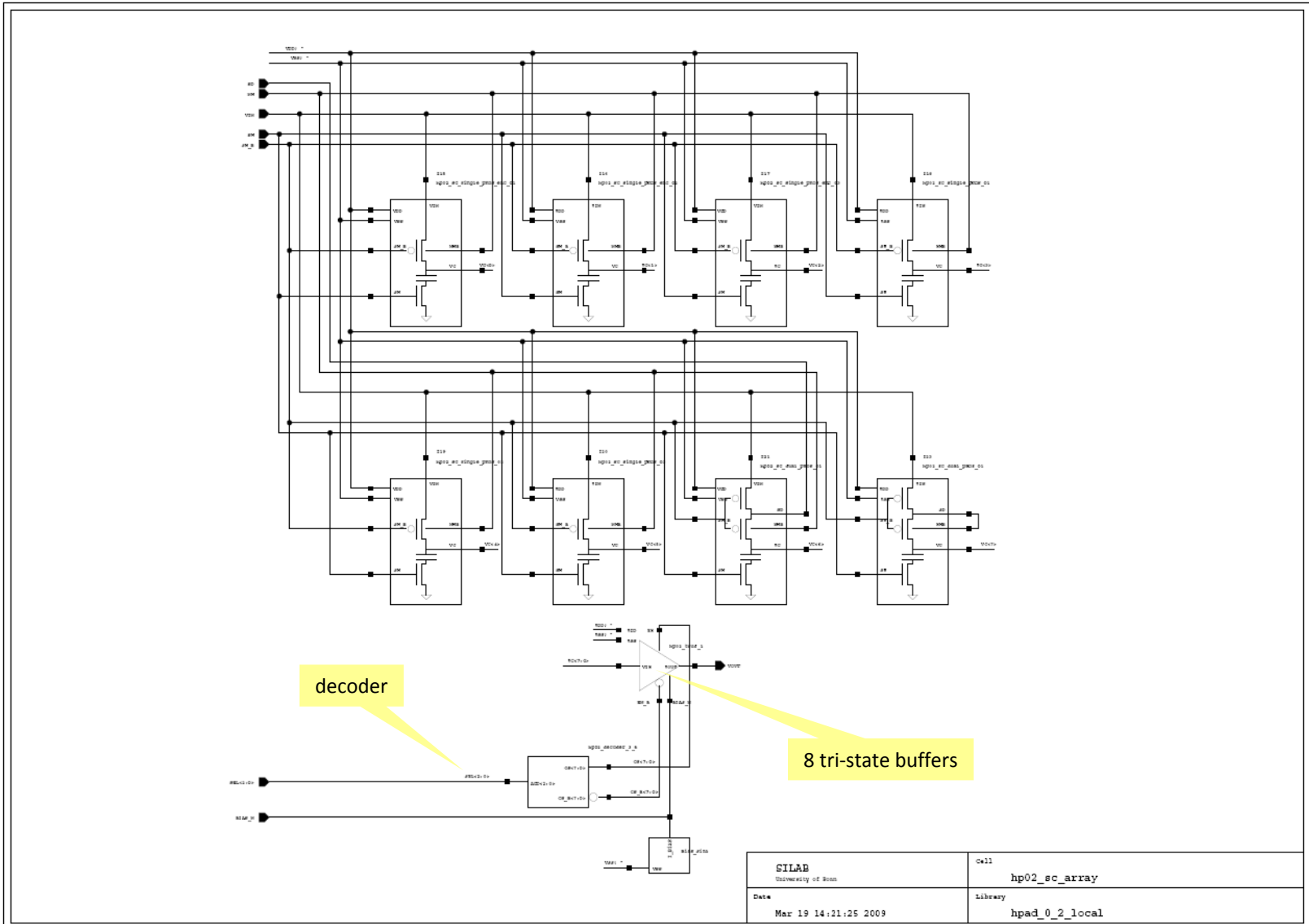

Towards the Analog Pipeline

- Analog memory test structure
 - 8 sampling cells
 - based on type 8 cell
(dual switch, linear I_{ppfet} , $W/L = 0.64/0.12$)

 
- Modifications
 - added **bottom plate switch** for all cells
 - V_{SD} floating
 - One cell with buffer at capacitor node
 - small **digital part** to generate **control signals**




Charge injection

- hard to compensate off-line if **signal dependent**
 - can be reduced to **constant offset** if switch source node sees a (low impedance) **constant voltage**
 - add **bottom plate switch**
- Write sequence
 - insert delay between top- and bottom plate switch off transition (switch off bottom first)
 - Read sequence
 - switch bus line to fixed potential (pre-charge V_{PRE})
 - switch on top plate first
 - KT/C noise ($C_s = 200$ fF): $V_{n_{KT/C}} = 100$ μ V

8-Cell Analog Pipeline Test Structure

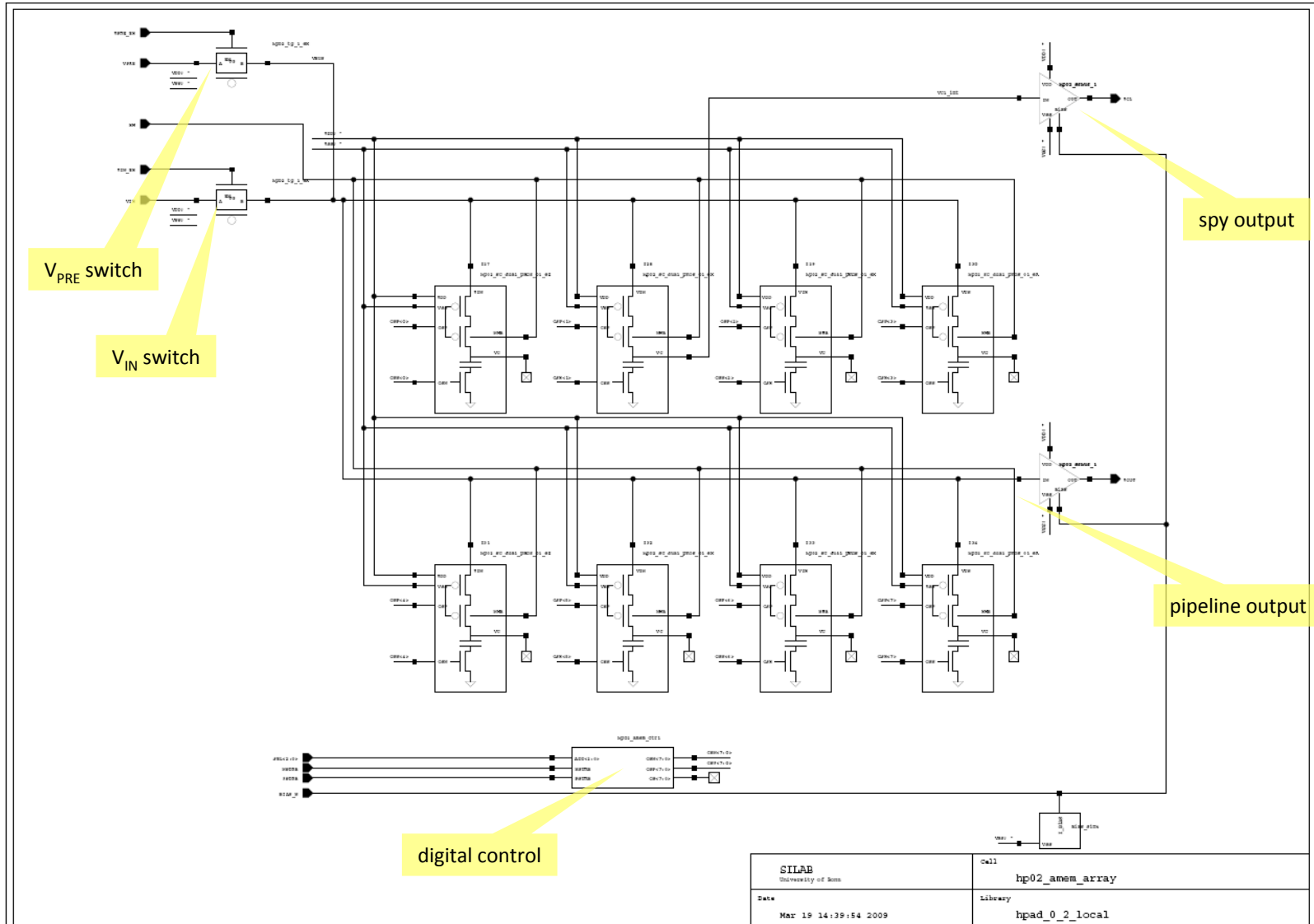

Analog Pipeline Test Structure - Layout

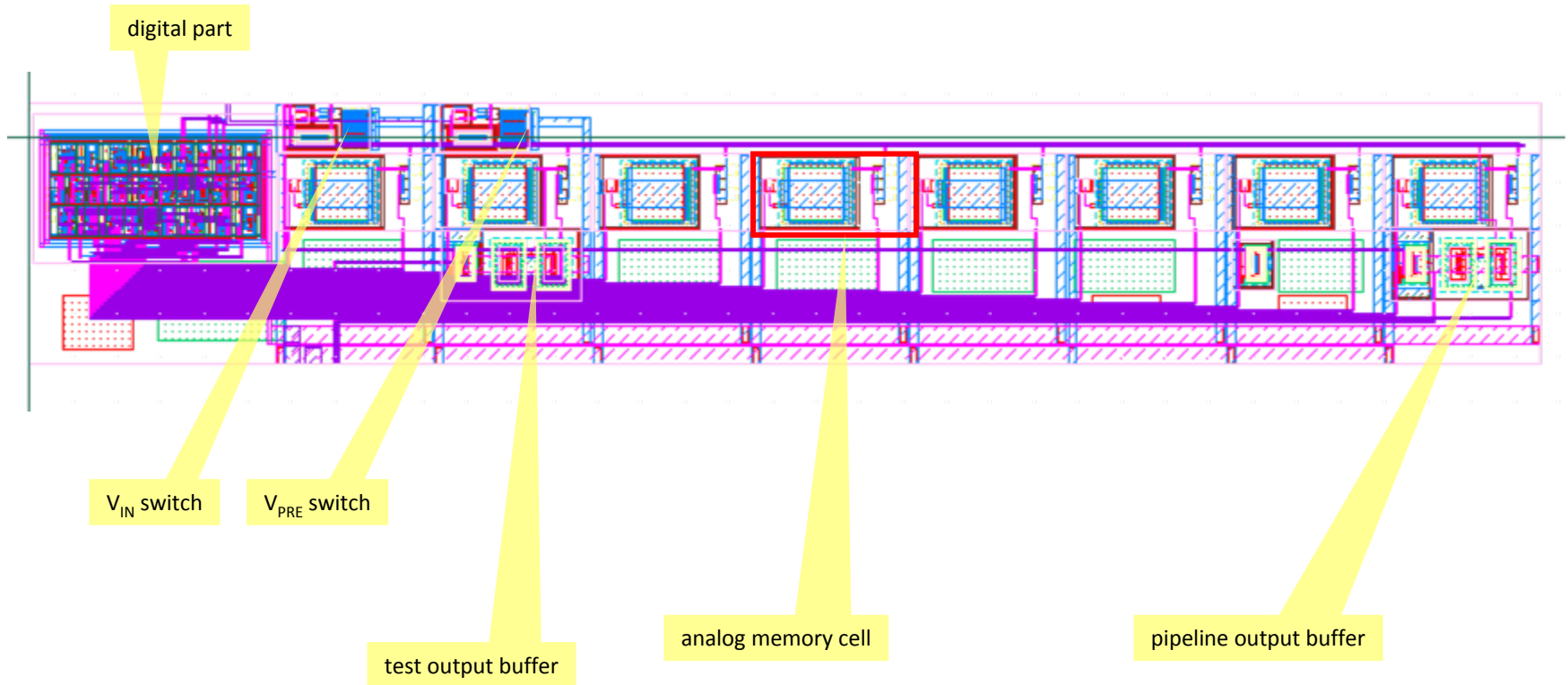


Analog Memory Cell – Layout Issues

Not area optimized!

- 200fF capacitance ($6\mu \cdot 6\mu$ *DGNCAP*)
- dual linear top plate switch (*PFET*)
- single enclosed bottom plate switch (*NFET*)

Estimation for optimized layout

- with *DGNCAP* ($\sim 10\text{fF}/\mu\text{m}^2$):
 - $10\mu \cdot 7\mu$ overall
 - 400 cells $\rightarrow (167\mu\text{m})^2$
 - need layout area for CSA, dig. control, dig. pipeline, buffer etc...
- with *MIMCAP* ($4.5\text{fF}/\mu\text{m}^2$): $12\mu \cdot 8\mu$ (cap only!)
 - still dominated by cap. area
 - no common bottom plate, low density layout rules for MIM layers
 - 400 cells $\rightarrow (195\mu\text{m})^2$
 - need to share layout area with C_F !

 

Analog Pipeline - Modes of Operation

- Write voltage, read voltage
 - voltage follower at the output, easy to implement
 - C_S does not have to be linear (use of *DGNCAP* ok)
 - read: sampled charge re-distributes on bus capacitance C_{PAR} and C_S
 - $C_S \gg C_{PAR}$ otherwise signal loss due to capacitive charge division
 - signal division tolerable?
- Write Voltage, read charge
 - CSA as output driver
 - output signal (almost) independent of C_{PAR}
 - needs linear C_S (*MIMCAP*)
- Write Charge, read charge
 - possible but more complicated switching sequence

Preparation of 16 x 16 pixel matrix design

- input dynamic range: $V_{\text{MIN}} > V_{\text{THR}}$ ($\sim 0,5\text{V}$, low power pmos switch)
- pixel driver: voltage buffer or CSA (switched capacitor, differential?)
- digital pipeline \rightarrow same as analog with smaller capacitor
- digital blocks
 - in-pixel control: memory cell select, write/read clocks
 - pixel selection: row/column select
- number of storage cells
- floorplan!

Some other Remarks

- A lot of measurement data of the HPAD 0.1 test structures has been produced
 - switch and capacitor arrays → parametric V-I curves
 - still some issues: are they (self) consistent?
 - **conclusions?**
- What is missing
 - DGNCAP pre- and after irradiation (capacitance and leakage)
 - results from OPA and alternative storage structures
- What about radiation with more realistic dose rates?
- General chip design issues
 - What is the status of the design of a radiation hard standard cell library?
 - What about enhanced pcells for enclosed fets (with added RX contacts)
 - fix bug in ASSURA extraction for enclosed layouts
 - Does anybody has experience with HERCULES LVS/DRC
- **Leakage performance of the non-irradiated switch still not shown**
- **rad-hard 'zero leakage' switch seem almost impossible → active compensation will help, but needs power and area**

